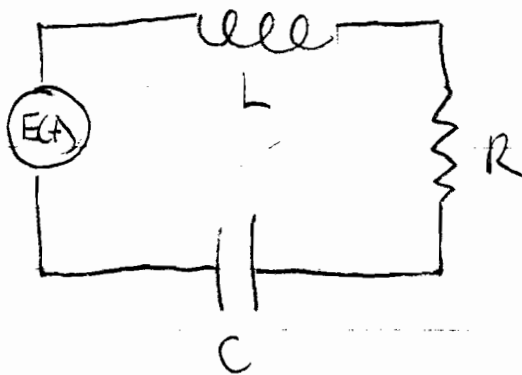


I Kirchoff's Law

$$E(t) - L \frac{di}{dt} - Ri - \frac{1}{C} q = 0$$

\uparrow \uparrow \uparrow
 voltage drops

$$\Rightarrow L \frac{di}{dt} + Ri + \frac{1}{C} q = E(t)$$

$$\Rightarrow \text{but } i = \frac{dq}{dt}$$

$$\Rightarrow \boxed{L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = E(t)}$$

$$L > 0$$

$$R > 0$$

$$C > 0$$

II Solution:

$$D = \frac{-R \pm \sqrt{R^2 - 4L/C}}{2L}$$

$$\text{if } R^2 - 4L/C \begin{cases} < 0 & \text{underdamped} \\ = 0 & \text{critically damped} \\ > 0 & \text{overdamped} \end{cases}$$

III. Comparison to VIBRATION PROBLEM

$$\begin{array}{ccccccc} L q'' & + & R q' & + & \frac{1}{C} q & = & E(t) \\ \updownarrow & \updownarrow & & & \updownarrow & & \updownarrow \\ m x'' & + & b x' & + & k x & = & F(t) \end{array}$$

i.e. this is the same problem mathematically, the application has changed, but the solution techniques are the same.